

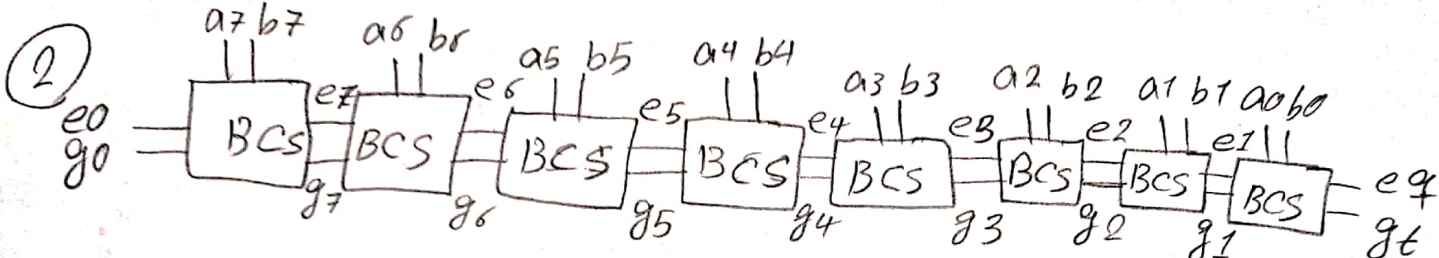


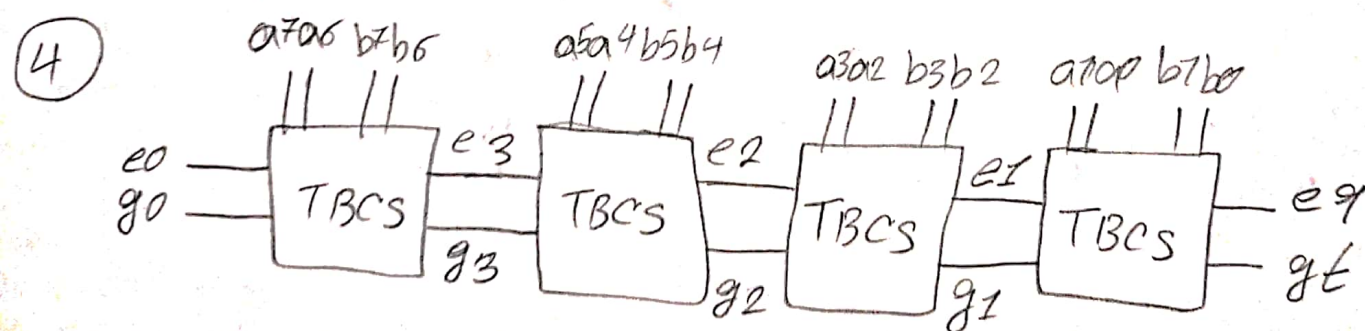① This assign statement calculate whether a is greater than b or not.



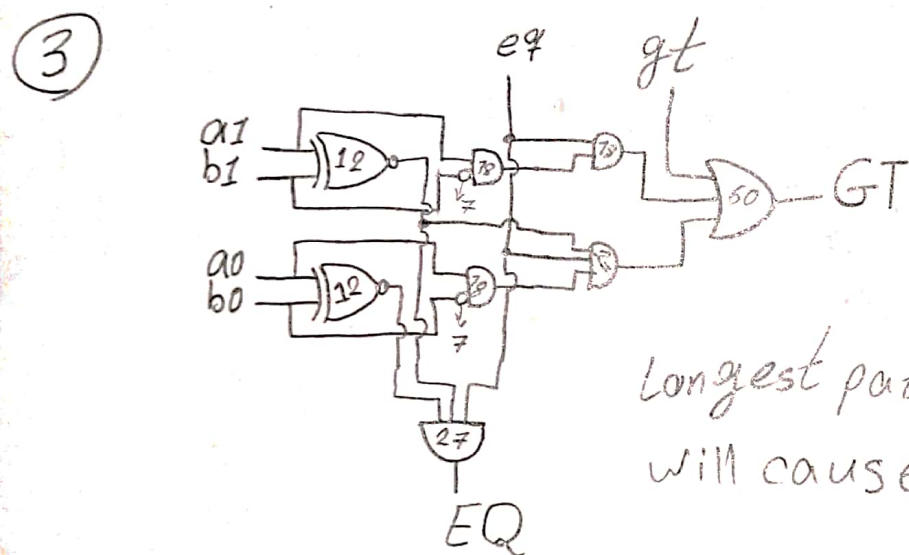we will see worst case delay in $a=0$ to $a=128$ which is 181ns.



we will see worst case delay in $a=0$ to $a=128$ which is 450ns.

⑤ The TBCS circuit has more delay.